

How do circuits work?

Fill in the missing words

Loop

Complete

Energy

Path

Positive

Electricity

Negative

A circuit is a _____ that allows _____ to pass through it.

Electricity always travels from the _____ to the _____.

A circuit will only work if it is _____. This means it must make a complete _____, otherwise the electrical _____ cannot flow.



Draw arrows on the diagram to show which way the electricity is flowing.